

# CS204: 數位系統設計

## Synchronous Sequential Logic

---

# Outline of Chapter 5

---

- ▣ 5.1 Introduction
- ▣ 5.2 Sequential Circuits
- ▣ 5.3 Storage Element: Latches
- ▣ 5.4 Storage Element: Flip-Flops
- ▣ 5.5 Analysis of Clocked Sequential Circuits
- ▣ **5.6 Synthesizable HDL Models of Sequential Circuits**
- ▣ 5.7 State Reduction and Assignment
- ▣ 5.8 Design Procedure

# Mealy and Moore models

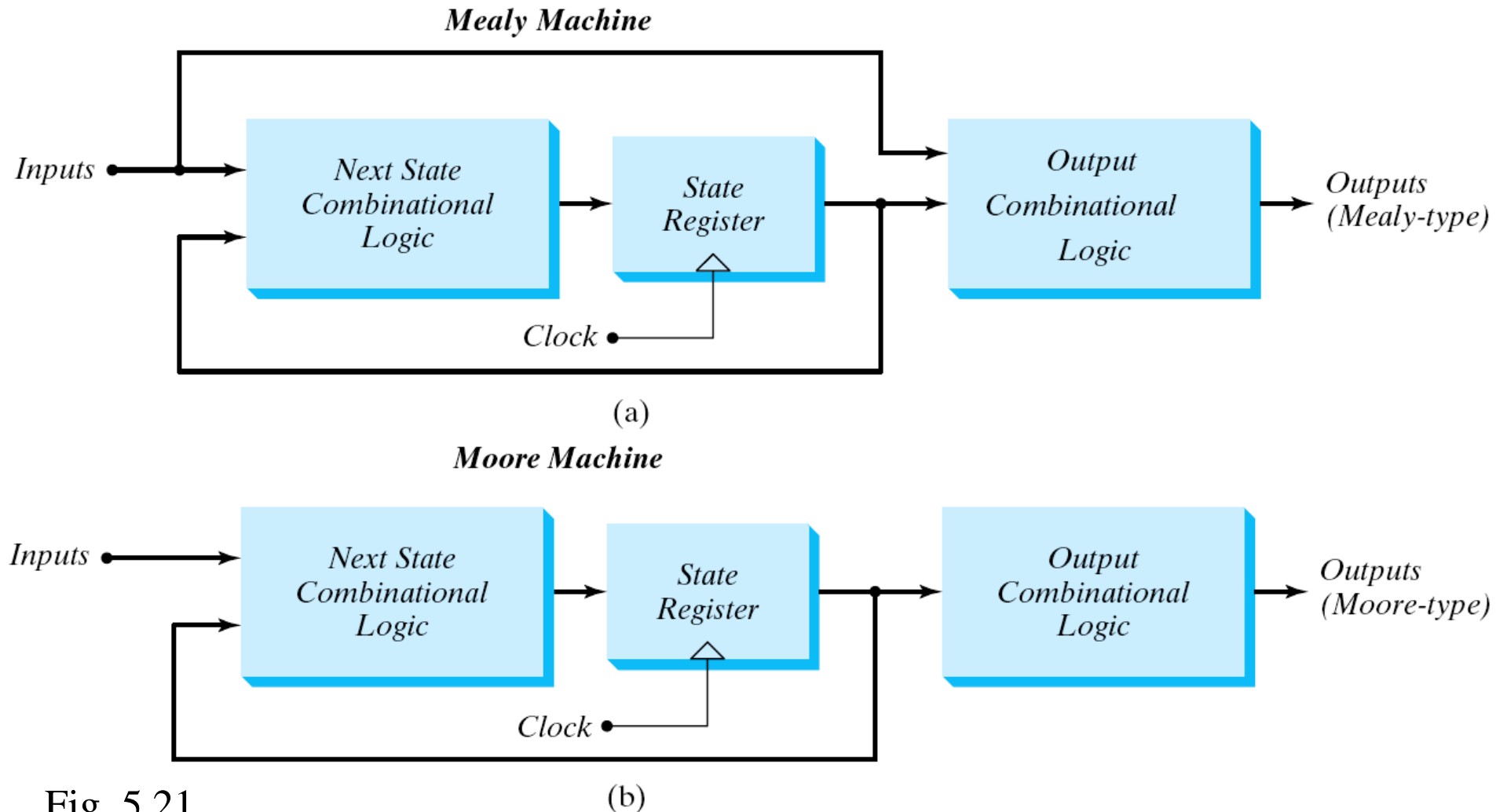


Fig. 5.21

Block diagram of Mealy and Moore state machine

# 5-7 Synthesizable HDL Models of Sequential Circuits

## ■ Behavioral Modeling

Example: Two ways to provide free-running clock

```
initial  
  begin  
    clock = 1'b0;  
    repeat (30)  
      #10 clock = ~clock;  
  end
```

```
initial  
  begin  
    clock = 1'b0;  
  end  
  
  initial 300 $finish;  
  always #10 clock = ~clock;
```

Example: Another way to describe free-running clock

```
initial begin clock = 0; forever #10 clock = ~clock; end
```

# Behavioral Modeling

**always** statement

```
always @ (event control expression) begin  
    // Procedural assignment statements that execute when the condition is met  
end
```

Examples:

```
always @ (A or B or C)
```

```
always @(posedge clock or negedge reset)    // Verilog 1995
```

```
always @(posedge clock, negedge reset)    // Verilog 2001, 2005
```

Two procedural blocking assignments:

```
B = A  
C = B + 1
```

Two nonblocking assignments:

```
B <= A  
C <= B + 1
```

# Flip-Flops and Latches

## ■ HDL Example 5.1

### HDL Example 5.1

---

// Description of D latch (See Fig. 5.6)

**module** D\_latch (Q, D, enable);

**output** Q;

**input** D, enable;

**reg** Q;

**always @** (enable **or** D)

**if** (enable) Q <= D;

    // Same as: **if** (enable == 1)

**endmodule**

// Alternative syntax (Verilog 2001, 2005)

**module** D\_latch (**output reg** Q, **input** enable, D);

**always @** (enable, D)

**if** (enable) Q <= D;

    // No action if *enable* not asserted

**endmodule**

---

# Flip-Flops and Latches

## ■ HDL Example 5.2

### HDL Example 5.2

---

```
// D flip-flop without reset
module D_FF (Q, D, Clk);
  output Q;
  input  D, Clk;
  reg    Q;
  always @ (posedge Clk)
    Q <= D;
endmodule
```

```
// D flip-flop with asynchronous reset (V2001, V2005)
module DFF (output reg Q, input D, Clk, rst);
  always @ (posedge Clk, negedge rst)
    if (~rst) Q <= 1'b0; // Same as: if (rst == 0)
    else Q <= D;
endmodule
```

---

# Characteristic Equation

$$Q(t + 1) = Q \oplus T$$



For a *T* flip-flop

$$Q(t + 1) = JQ' + K'Q$$



For a *JK* flip-flop

## ■ HDL Example 5.3

### HDL Example 5.3

---

```
// T flip-flop from D flip-flop and gates
module TFF (Q, T, Clk, rst);
    output Q;
    input  T, Clk, rst;
    wire   DT;
    assign DT = Q ^ T ;           // Continuous assignment
    // Instantiate the D flip-flop
    DFF TF1 (Q, DT, Clk, rst);
endmodule
```



# HDL Example 5-3 (Continued)

```
// JK flip-flop from D flip-flop and gates (V2001, 2005)
module JKFF (output reg Q, input J, K, Clk, rst);
    wire JK;
    assign JK = (J & ~Q) | (~K & Q);
    // Instantiate D flip-flop
    DFF JK1 (Q, J, K, Clk, rst);
endmodule

// D flip-flop (V2001, V2005)
module DFF (output reg Q, input D, Clk, rst);
    always @ (posedge Clk, negedge rst)
        if (~rst) Q <= 1'b0;
        else Q <= D;
endmodule
```

---

# HDL Example 5-4

- Functional description of JK flip-flop

## HDL Example 5.4

---

```
// Functional description of JK flip-flop (V2001, 2005)
module JK_FF (input J, K, Clk, output reg Q, output Q_b);
    assign Q_b = ~ Q ;
    always @ (posedge Clk)
        case ({J,K})
            2'b00: Q <= Q;
            2'b01: Q <= 1'b0;
            2'b10: Q <= 1'b1;
            2'b11: Q <= ~Q;
        endcase
endmodule
```

---

# State Diagram

## ■ HDL Example 5.5: Mealy HDL model

### HDL Example 5.5

---

// Mealy FSM zero detector (See Fig. 5.16)

Verilog 2001, 2005 syntax

**module** Mealy\_Zero\_Detector (

**output reg** y\_out,

**input**      x\_in, clock, reset

);

**reg** [1: 0]      state, next\_state;

**parameter**      S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

**always @ (posedge clock, negedge reset)**  Verilog 2001, 2005 syntax

  if (reset == 0) state <= S0;

**else** state <= next\_state;

# HDL Example 5-5 (Continued)

```
always @ (state, x_in)                                // Form the next state
  case (state)
    S0:      if (x_in) next_state = S1; else next_state = S0;
    S1:      if (x_in) next_state = S3; else next_state = S0;
    S2:      if (~x_in) next_state = S0; else next_state = S2;
    S3:      if (x_in) next_state = S2; else next_state = S0;
  endcase

always @ (state, x_in)                                // Form the output
  case (state)
    S0:      y_out = 0;
    S1, S2, S3: y_out = ~x_in;
  endcase
endmodule

module t_Mealy_Zero_Detector;
  wire  t_y_out;
  reg    t_x_in, t_clock, t_reset;

  Mealy_Zero_Detector M0 (t_y_out, t_x_in, t_clock, t_reset);
  initial #200 $finish;
  initial begin t_clock = 0; forever #5 t_clock = ~t_clock; end
```

# HDL Example 5-5 (Continued)

**initial fork**

```
t_reset = 0;  
#2 t_reset = 1;  
#87 t_reset = 0;  
#89 t_reset = 1;  
#10 t_x_in = 1;  
#30 t_x_in = 0;  
#40 t_x_in = 1;  
#50 t_x_in = 0;  
#52 t_x_in = 1;  
#54 t_x_in = 0;  
#70 t_x_in = 1;  
#80 t_x_in = 1;  
#70 t_x_in = 0;  
#90 t_x_in = 1;  
#100 t_x_in = 0;  
#120 t_x_in = 1;  
#160 t_x_in = 0;  
#170 t_x_in = 1;
```

**join**

**endmodule**

# Mealy\_Zero\_Detector

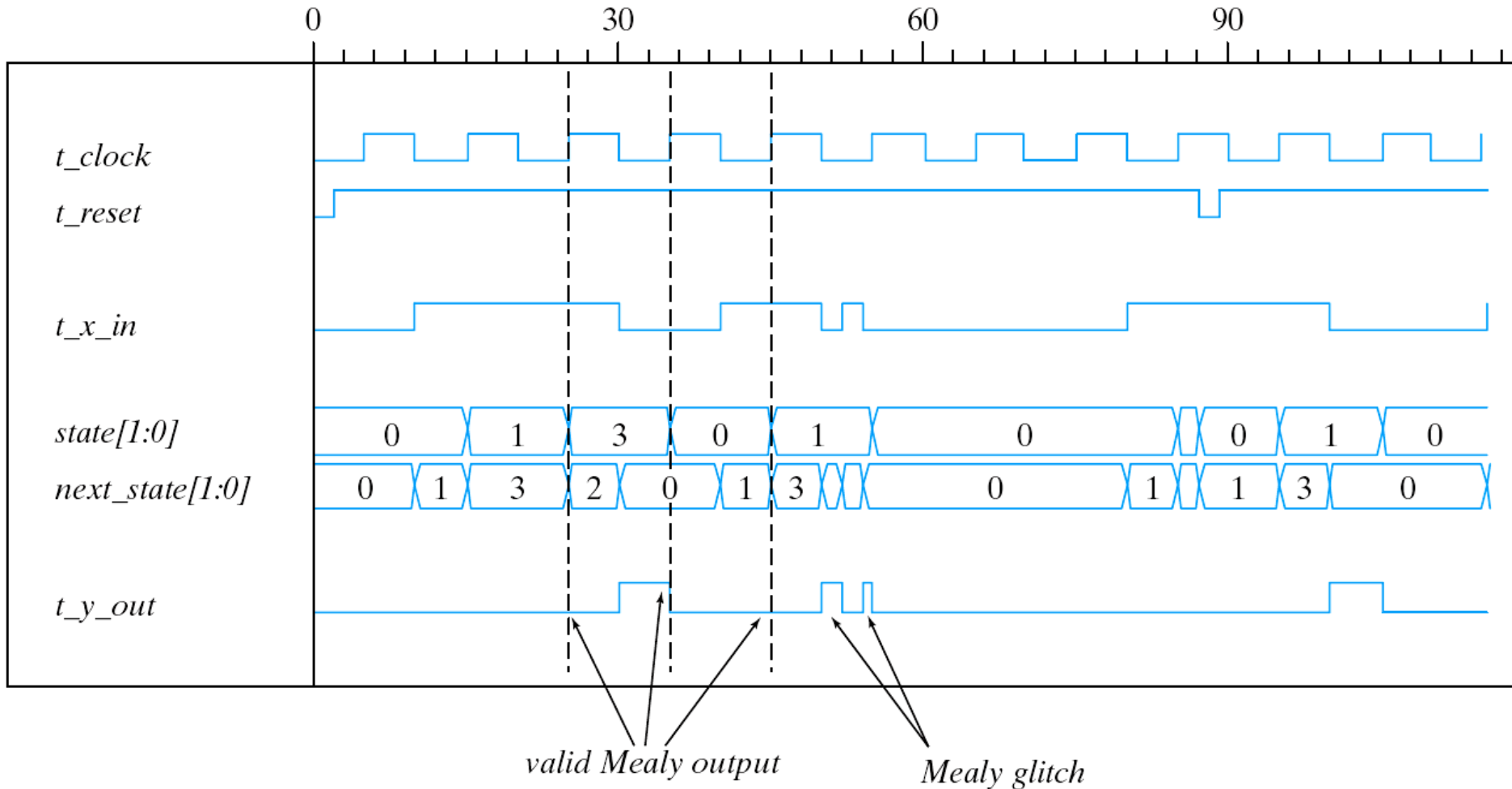


Fig. 5.22 Simulation output of *Mealy\_Zero\_Detector*

# HDL Example 5-6: Moore Model FSM

## HDL Example 5.6

```
// Moore model FSM (see Fig. 5.19)                                Verilog 2001, 2005 syntax
module Moore_Model_Fig_5_19 (
    output [1: 0]          y_out,
    input                x_in, clock, reset
);
    reg [1: 0]            state;
    parameter            S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

    always @ (posedge clock, negedge reset)
        if (reset == 0) state <= S0;                                // Initialize to state S0
        else case (state)
            S0:    if (~x_in) state <= S1; else state <= S0;
            S1:    if (x_in)  state <= S2; else state <= S3;
            S2:    if (~x_in) state <= S3; else state <= S2;
            S3:    if (~x_in) state <= S0; else state <= S3;
        endcase

    assign y_out = state;    // Output of flip-flops

endmodule
```

# Simulation Output of HDL Example 5-6

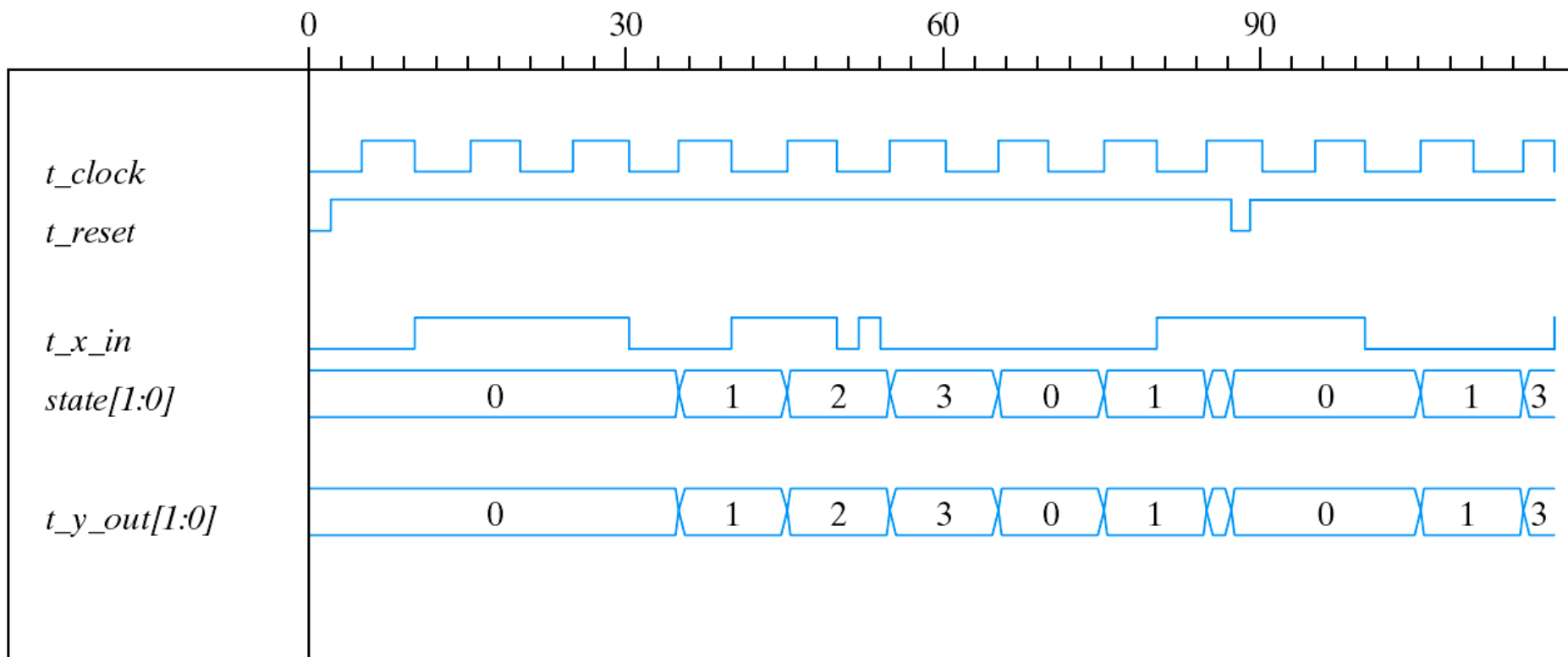


Fig. 5.23 Simulation output of HDL Example 5.6



# Structural Description of Clocked Sequential Circuits

## ■ HDL Example 5.7: State-diagram-based model

### HDL Example 5.7

---

```
// State-diagram-based model (V2001, 2005)
module Moore_Model_Fig_5_20 (
    output y_out,
    input  x_in, clock, reset
);
    reg [1: 0]          state;
    parameter          S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
    always @ (posedge clock, negedge reset)
        if (reset == 0) state <= S0;                // Initialize to state S0
        else case (state)
            S0:   if (x_in) state <= S1; else state <= S0;
            S1:   if (x_in) state <= S2; else state <= S1;
```

# HDL Example 5-7 (Continued)

```
S2:  if (x_in) state <= S3; else state <= S2;
S3:  if (x_in) state <= S0; else state <= S3;
endcase

assign y_out = (state == S3);           // Output of flip-flops
endmodule

// structural model
module Moore_Model_STR_Fig_5_20 (
    output  y_out, A, B,
    input   x_in, clock, reset
);
    wire    TA, TB;

    // Flip-flop input equations
    assign TA = x_in & B;
    assign TB = x_in;
    // Output equation
    assign y_out = A & B;
```

# HDL Example 5-7 (Continued)

```
// Instantiate Toggle flip-flops
Toggle_flip_flop_3 M_A (A, TA, clock, reset);
Toggle_flip_flop_3 M_B (B, TB, clock, reset);
endmodule

module Toggle_flip_flop (Q, T, CLK, RST_b);
    output    Q;
    input     T, CLK, RST_b;
    reg       Q;

    always @ (posedge CLK, negedge RST_b)
        if (RST_b == 0) Q <= 1'b0;
        else if (T) Q <= ~Q;
endmodule

// Alternative model using characteristic equation
// module Toggle_flip_flop (Q, T, CLK, RST_b);
// output    Q;
// input     T, CLK, RST_b;
// reg       Q;
```

# HDL Example 5-7 (Continued)

```
// always @ (posedge CLK, negedge RST)
//   if (RST_b == 0) Q <= 1'b0;
//   else Q <= Q ^ T;
// endmodule
```

```
module t_Moore_Fig_5_20;
```

```
  wire          t_y_out_2, t_y_out_1;
```

```
  reg           t_x_in, t_clock, t_reset;
```

```
  Moore_Model_Fig_5_20          M1(t_y_out_1, t_x_in, t_clock, t_reset);
```

```
  Moore_Model_STR_Fig_5_20      M2 (t_y_out_2, A, B, t_x_in, t_clock, t_reset);
```

# HDL Example 5-7 (Continued)

```
initial #200 $finish;
initial begin
    t_reset = 0;
    t_clock = 0;
    #5 t_reset = 1;
    repeat (16)
        #5 t_clock = ~t_clock;
    end
    initial begin
        t_x_in = 0;
        #15 t_x_in = 1;
        repeat (8)
            #10 t_x_in = ~t_x_in;
        end
    end
endmodule
```

---

# Simulation Output of HDL Example 5-7

 


Fig. 5.24 Simulation output of HDL Example 5.7