

CS204: 數位系統設計

Memory and Programmable Logic

Outline of Chapter 7

- ▣ 7.1 Introduction
- ▣ 7.2 Random-Access Memory
- ▣ 7.3 Memory Decoding
- ▣ 7.4 Error Detection and Correction
- ▣ 7.5 Read-Only Memory
- ▣ 7.6 Programmable Logic Array
- ▣ 7.7 Programmable Array Logic
- ▣ 7.8 Sequential Programmable Devices

7-1 Introduction (p.315)

▣ Memory

- ◆ Information storage
- ◆ A collection of cells store binary information

▣ RAM – Random-Access Memory

- ◆ Read operation
- ◆ Write operation


▣ ROM – Read-Only Memory

- ◆ Read operation only
- ◆ A programmable logic device


Programmable Logic Device (p.316)

■ Programmable Logic Device (PLD)

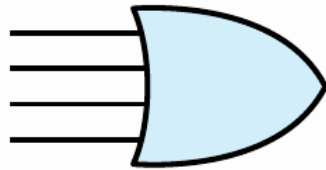- ◆ ROM – read only memory
- ◆ PLA – programmable logic array
- ◆ PAL – programmable array logic
- ◆ FPGA – field-programmable gate array
 - » programmable logic blocks
 - » programmable interconnects



(a) Conventional symbol

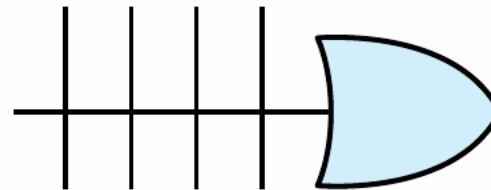

(b) Array logic symbol

Fig. 7.1 Conventional and array logic diagrams for OR gates

7-2 Random-Access Memory (p.317)

■ A memory unit

- ◆ Stores binary information in groups of bits (words)
- ◆ 8 bits (1 byte), 2 bytes, 4 bytes

■ Block diagram

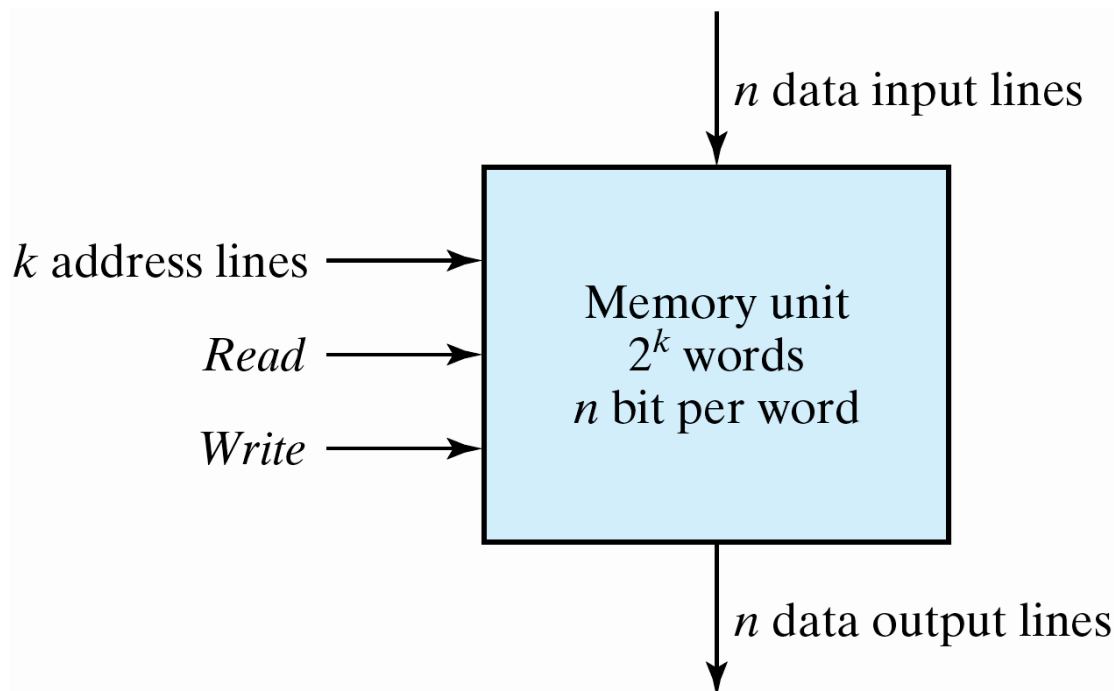


Fig. 7.2 Block diagrams of a memory unit

Example: 1024×16 Memory (p.318)

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 7.3 Contents of a 1024×16 memory

Write and Read Operations (p.319)

□ Write operation

- Apply the binary address to the address lines
- Apply the data bits to the data input lines
- Activate the *write* input

□ Read operation

- Apply the binary address to the address lines
- Activate the *read* input

Table 7.1

Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

Timing Waveforms (p.320)

- The operation of the memory unit is controlled by an external device
- The memory **access time**
 - ◆ the time required to select a word and **read** it
- The memory **cycle time**
 - ◆ the time required to complete a **write** operation
- Read and write operations must be synchronized with a clock
 - ◆ Usually, CPU clock cycle time < memory access/cycle time
 - ◆ Multiple CPU clock cycles for a memory operation
 - » A fixed number of CPU clock cycles

Memory Write Cycle (p.321)

- ◆ CPU clock – 50 MHz
- ◆ Memory access/cycle time < 50 ns


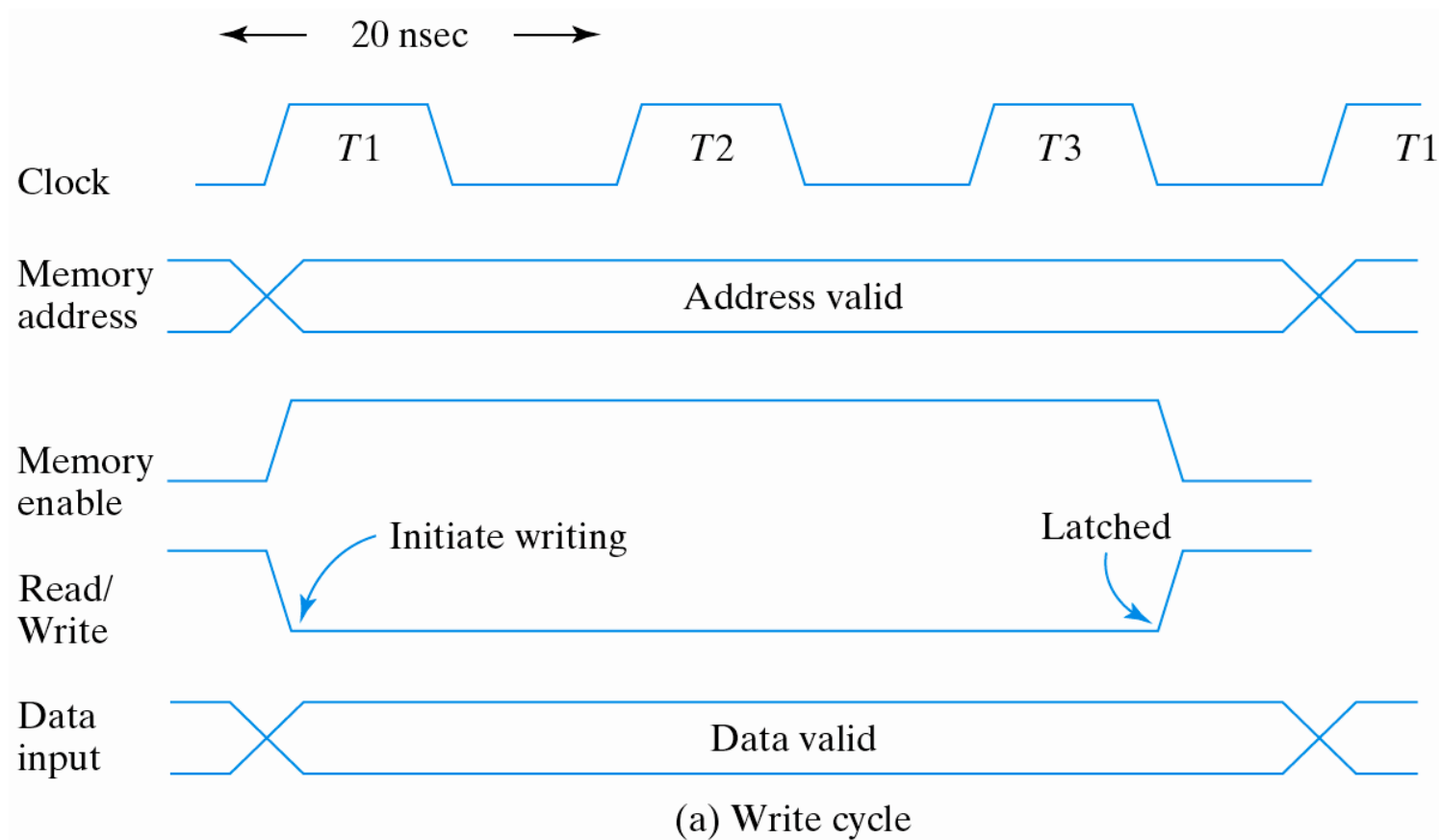


Fig. 7.4 Memory cycle timing waveforms

Memory Read Cycle (p.321)

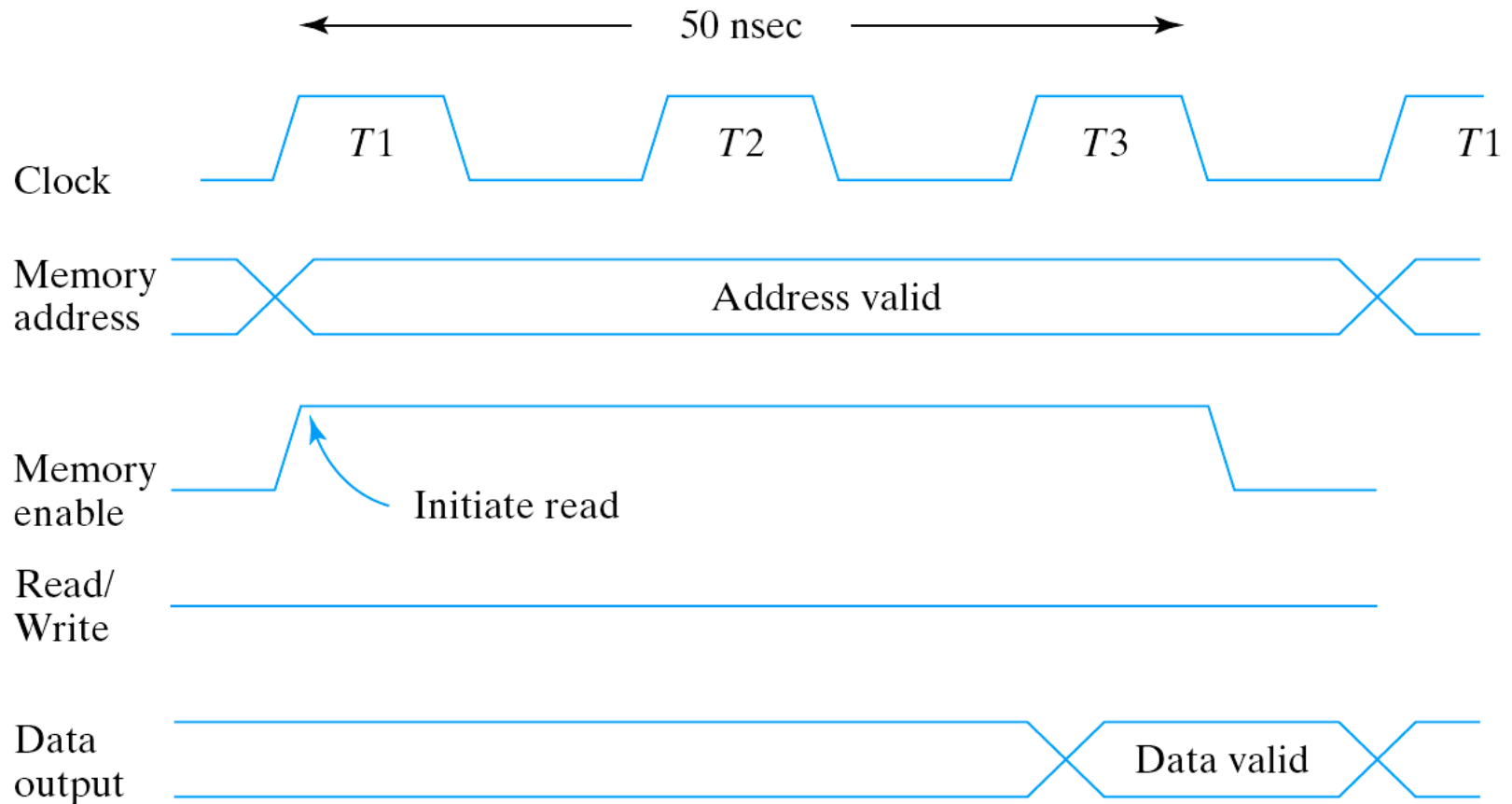

(b) Read cycle

Fig. 7.4 Memory cycle timing waveforms

Types of Memories (1/2) (p.322)

■ Random-access memory – RAM

- ◆ Access time is the same regardless the data location
- ◆ Cp.: hard disk, CD-ROM, DVD-ROM, tape (sequential access)

■ Static memory – SRAM

- ◆ Information is stored in latches
- ◆ Remains valid as long as power is applied
- ◆ Short read/write cycle

■ Dynamic memory – DRAM

- ◆ Information are stored in the form of charges on capacitors
- ◆ The stored charge tends to discharge with time
- ◆ Need to be **refreshed** (read and write back)
- ◆ Reduced power consumption
- ◆ Larger memory capacity

Types of Memories (2/2) (p.322)

▣ Volatile

- ◆ Lose stored information when power is turned off
- ◆ SRAM, DRAM


▣ Non-volatile

- ◆ Retains its stored information after the removal of power
- ◆ ROM
- ◆ EPROM, EEPROM
 - » Erasable Programmable ROM, Electrically Erasable Programmable ROM
- ◆ Flash memory

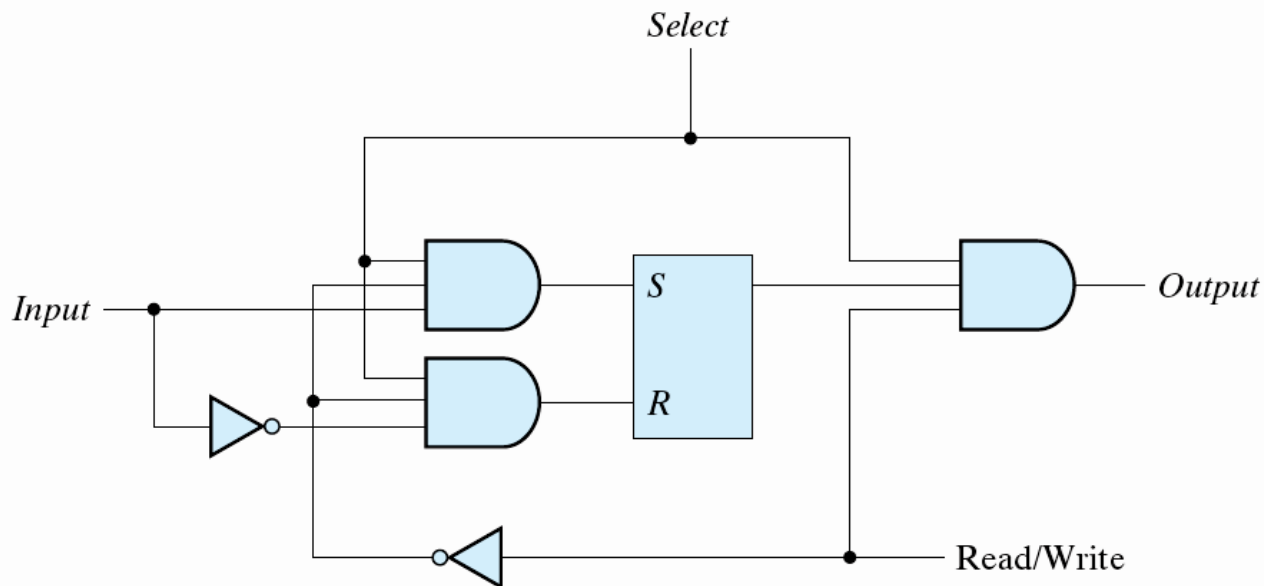
7-3 Memory Decoding (p.323)

■ A memory unit

- ◆ The storage components
- ◆ The decoding circuits to select the memory word



(a) Logic diagram

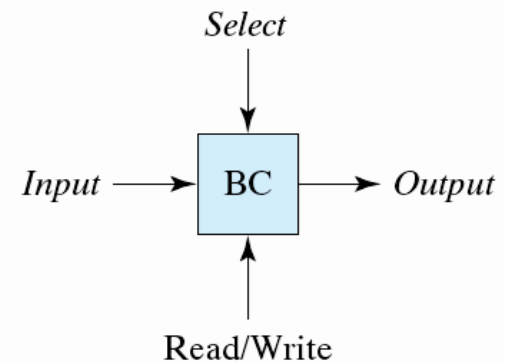

(b) Block diagram

Fig. 7.5 Memory cell (equivalent logic)

Internal Construction (p.324)

■ A RAM of m words and n bits per word

- ◆ $m \times n$ binary storage cells
- ◆ Decoding circuits to select individual words
 - » k -to- 2^k decoder

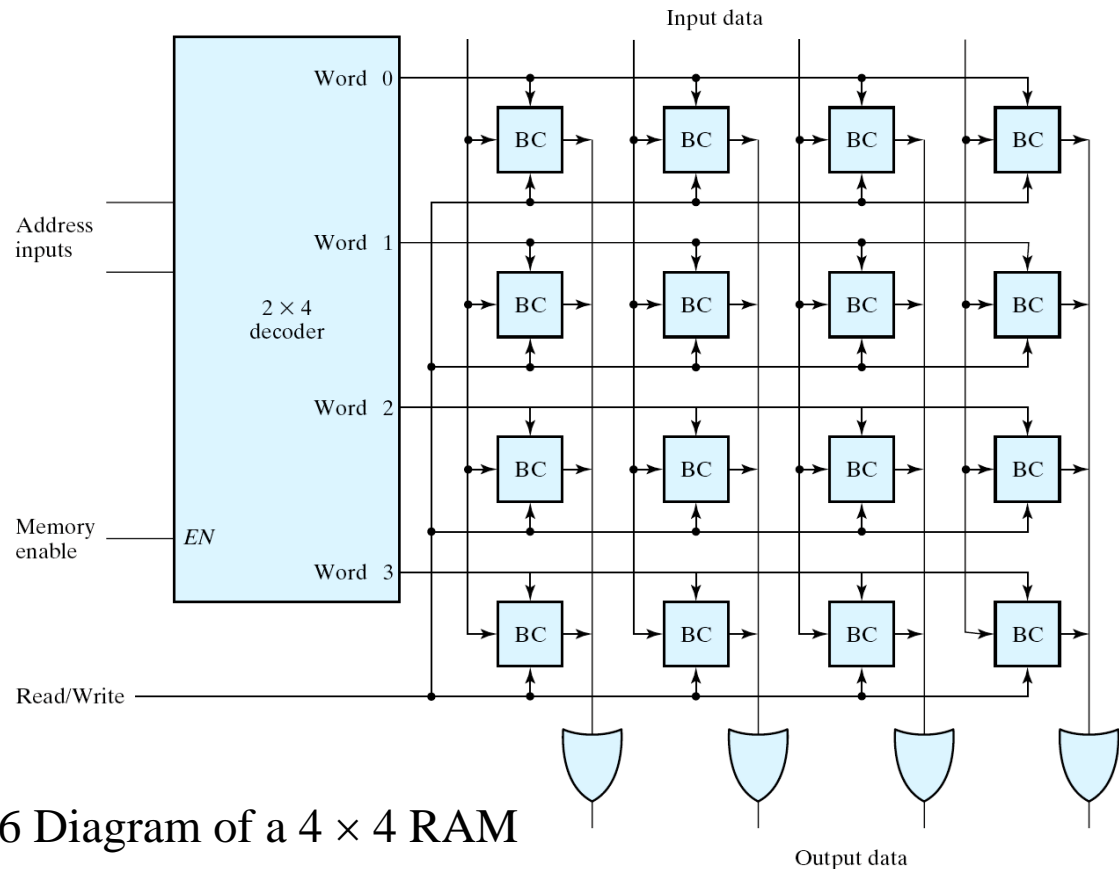


Fig. 7.6 Diagram of a 4 × 4 RAM

Coincident Decoding (1/2) (p.325)

- A two-dimensional selection scheme
 - ◆ Reduce the complexity of the decoding circuits

- A 10-to-1024 decoder
 - ◆ 1024 AND gates with 10 inputs per gates

- **Alternative:** Two 5-to-32 decoders
 - ◆ 2 * (32 AND gates with 5 inputs per gates)
 - ◆ Reduce the circuit complexity and the cycle time

Coincident Decoding (2/2) (p.326)

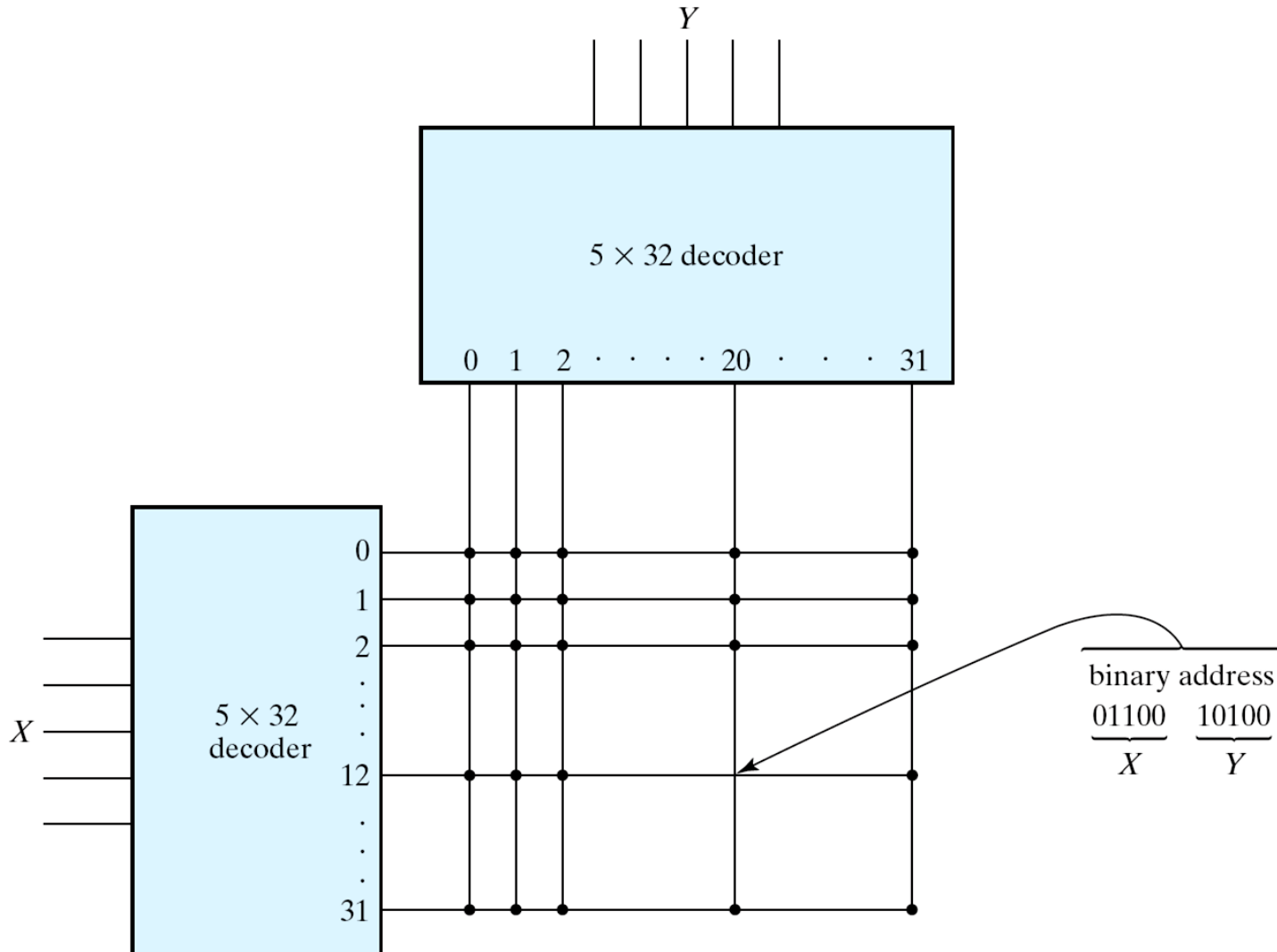


Fig. 7.7 Two-dimensional decoding structure for a 1K-word memory

Address Multiplexing (1/2) (p.327)

- To reduce the number of pins in the IC package
 - ◆ consider a 64M×1 DRAM
 - » 26-bit address lines
 - ◆ Multiplex the address lines in one set of address input pins
 - ◆ RAS – row address strobe
 - ◆ CAS – column address strobe

Address Multiplexing (2/2) (p.327)

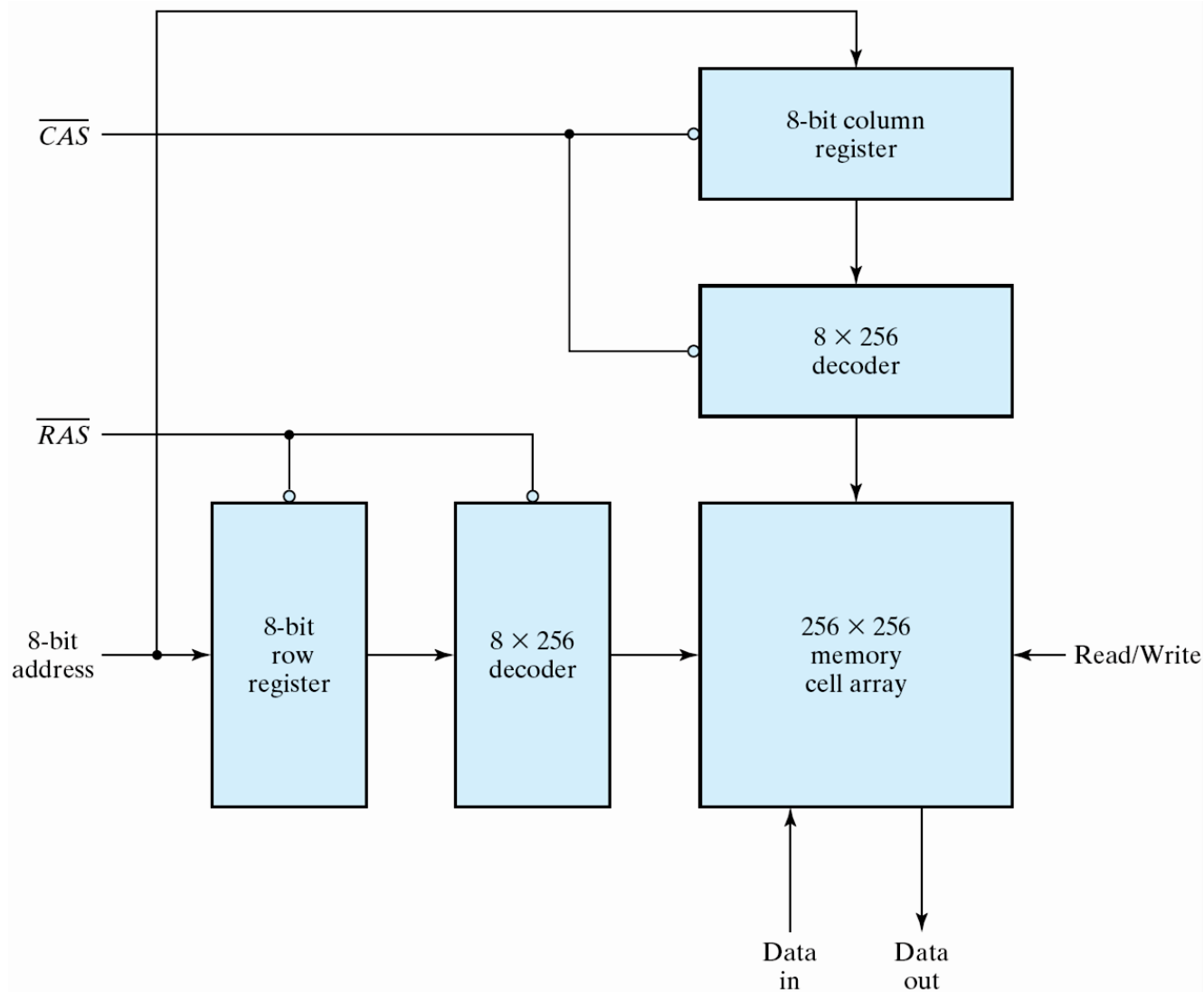


Fig. 7.8 Address multiplexing for a 64K DRAM

7-5 Read-Only Memory (p.331)

- ▣ Store permanent binary information

- ▣ $2^k \times n$ ROM

- ◆ k address input lines
- ◆ Enable input(s) (optional)
- ◆ Three-state outputs (optional)

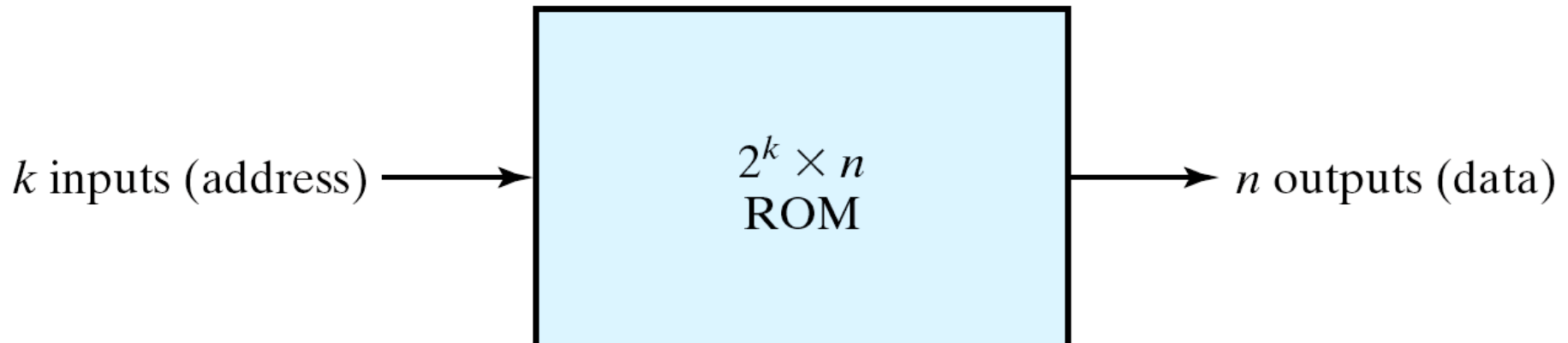


Fig. 7.9 ROM block diagram

Internal Logic of a 32×8 ROM (p.332)

- ◆ 5-to-32 decoder
- ◆ 8 OR gates
 - » Each has 32 inputs
- ◆ 32×8 internal programmable connections

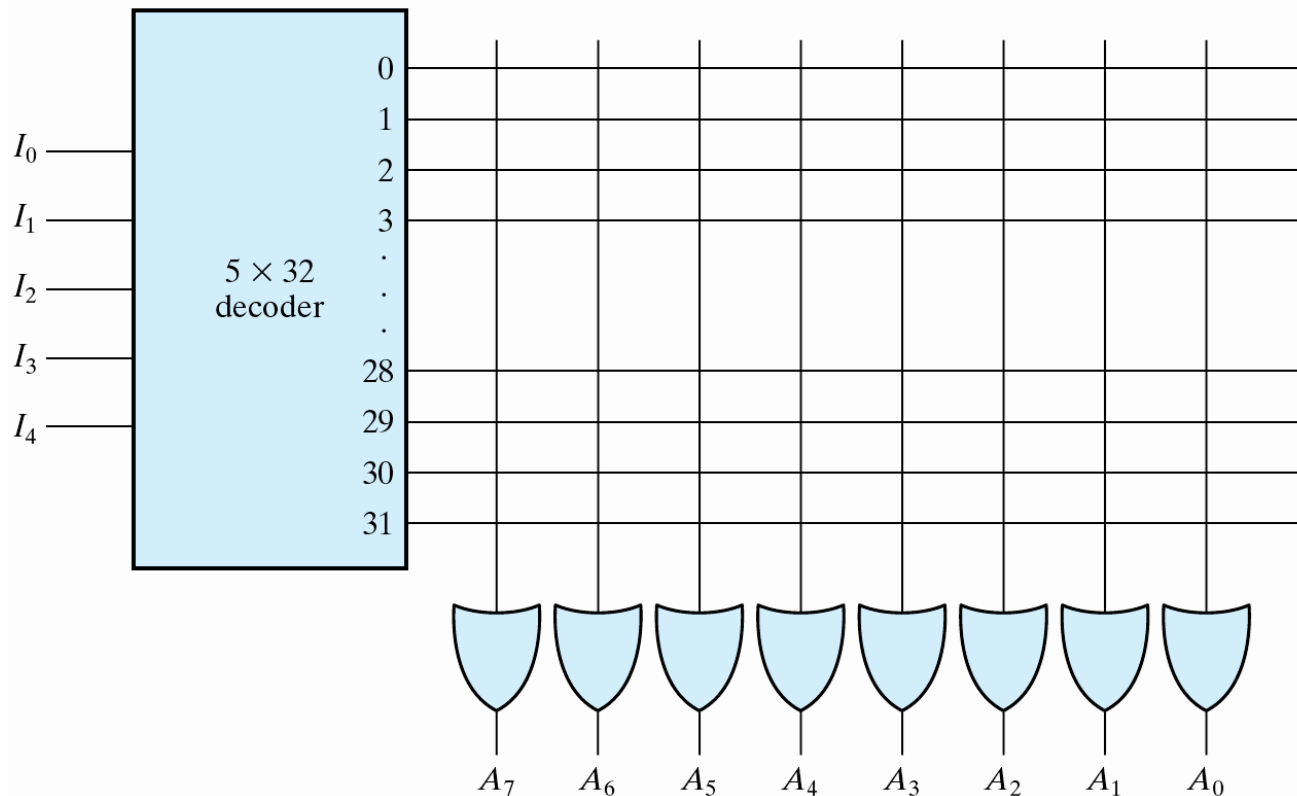


Fig. 7.10 Internal logic of a 32×8 ROM

Programming a ROM (p.333, 334)

□ Programmable interconnections

◆ Crosspoint switch


» Each "fuse" can be blown (**opened**) by applying a high voltage pulse

◆ Close (two lines are connected)

◆ Open (two lines are disconnected)

Table 7.3
ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮						⋮				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

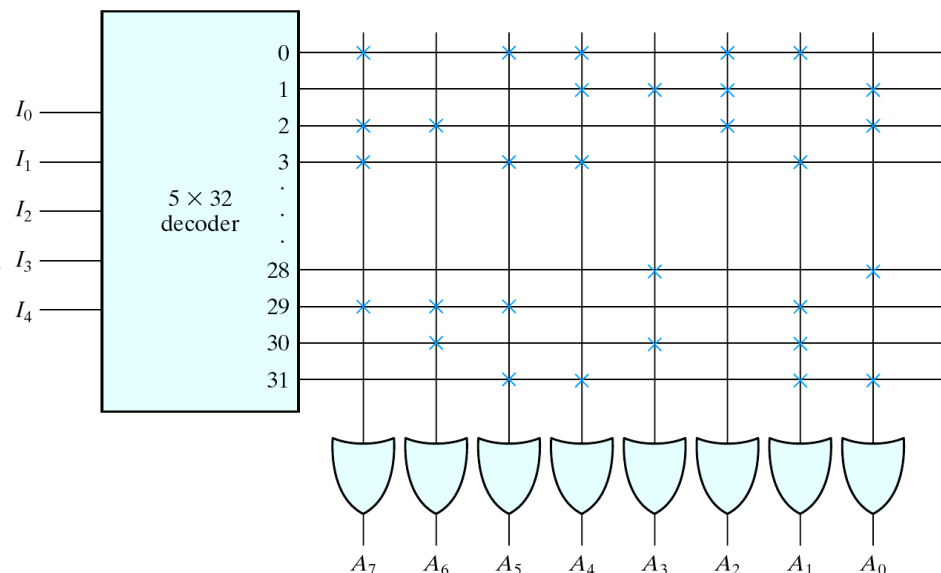

Combinational Circuit Implementation

(p.334)

▣ ROM: a decoder + OR gates

- ◆ Boolean function = sum of minterms
- ◆ For an n -input, m -output combinational circuit
 $\Rightarrow 2^n \times m$ ROM

▣ Design procedure:

1. Determine the **size of ROM**
2. Obtain the programming **truth table** of the ROM
3. The truth table = the **fuse** pattern

Three-Bit Binary Square (1/2) (p.335)


Table 7.4

Truth Table for Circuit of Example 7.1

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

- ◆ 3 inputs, 6 outputs
- ◆ $B_1 = 0$
- ◆ $B_0 = A_0$
- ◆ Use 8x4 ROM

Three-Bit Binary Square (2/2) (p.335)

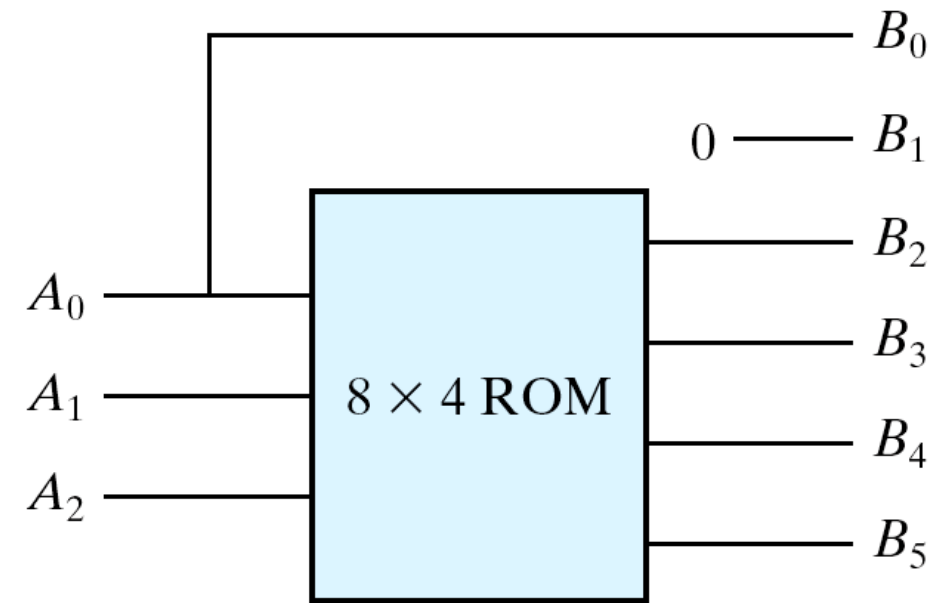

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 7.12 ROM implementation of Example 7.1

Types of ROMs (p.336)


▣ Types of ROM

- ◆ Mask programming ROM
 - » IC manufacturers, economical only if large quantities
- ◆ PROM: Programmable ROM
 - » Fuses, one-time program
- ◆ EPROM: erasable PROM
 - » Floating gate
 - » Ultraviolet light erasable
- ◆ EEPROM: electrically erasable PROM
 - » E²PROM
- ◆ Flash ROM
 - » Widespread applications in recent years
 - » Limited times of write operations $\sim 10^5$ erase cycles


Combinational PLDs (p.337)

Three major types of combinational PLD


AND-OR array

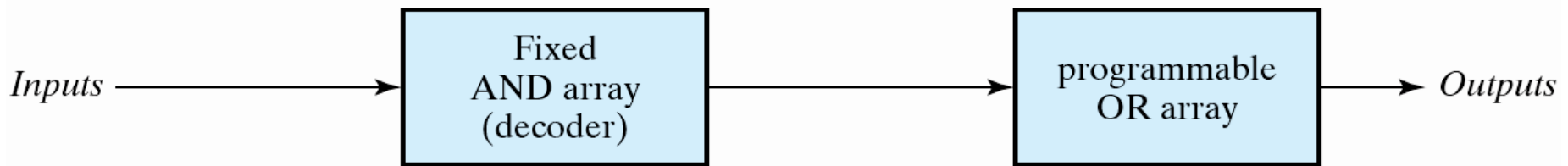

(a) Programmable read-only memory (PROM)

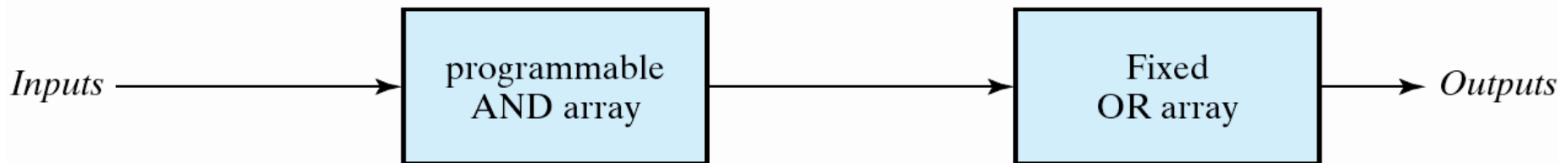

(b) Programmable array logic (PAL)

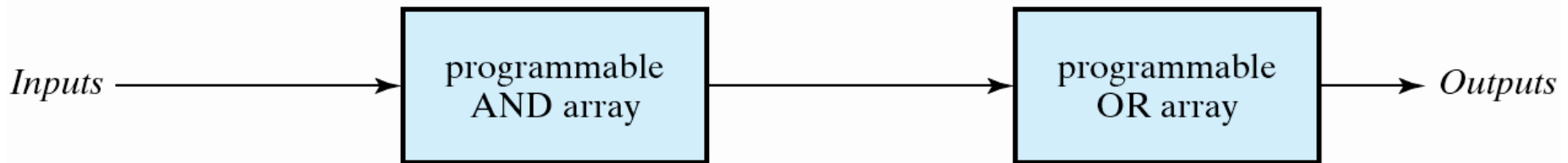

(c) Programmable logic array (PLA)

Fig. 7.13 Basic configuration of three PLDs

7.6 Programmable Logic Array (p.337)

■ Programmable Logic Array – PLA

- ◆ An array of programmable AND gates
 - » Capable of generating any product term
- ◆ An array of programmable OR gates
 - » Capable of generating sum of the products
- ◆ XOR gate at the output
 - » Capable of generating positive and negative phases
- ◆ More flexible than ROM
- ◆ Use less circuits than ROM
 - » Generate required product terms

PLA Implementation (1/2) (p.338, 339)

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

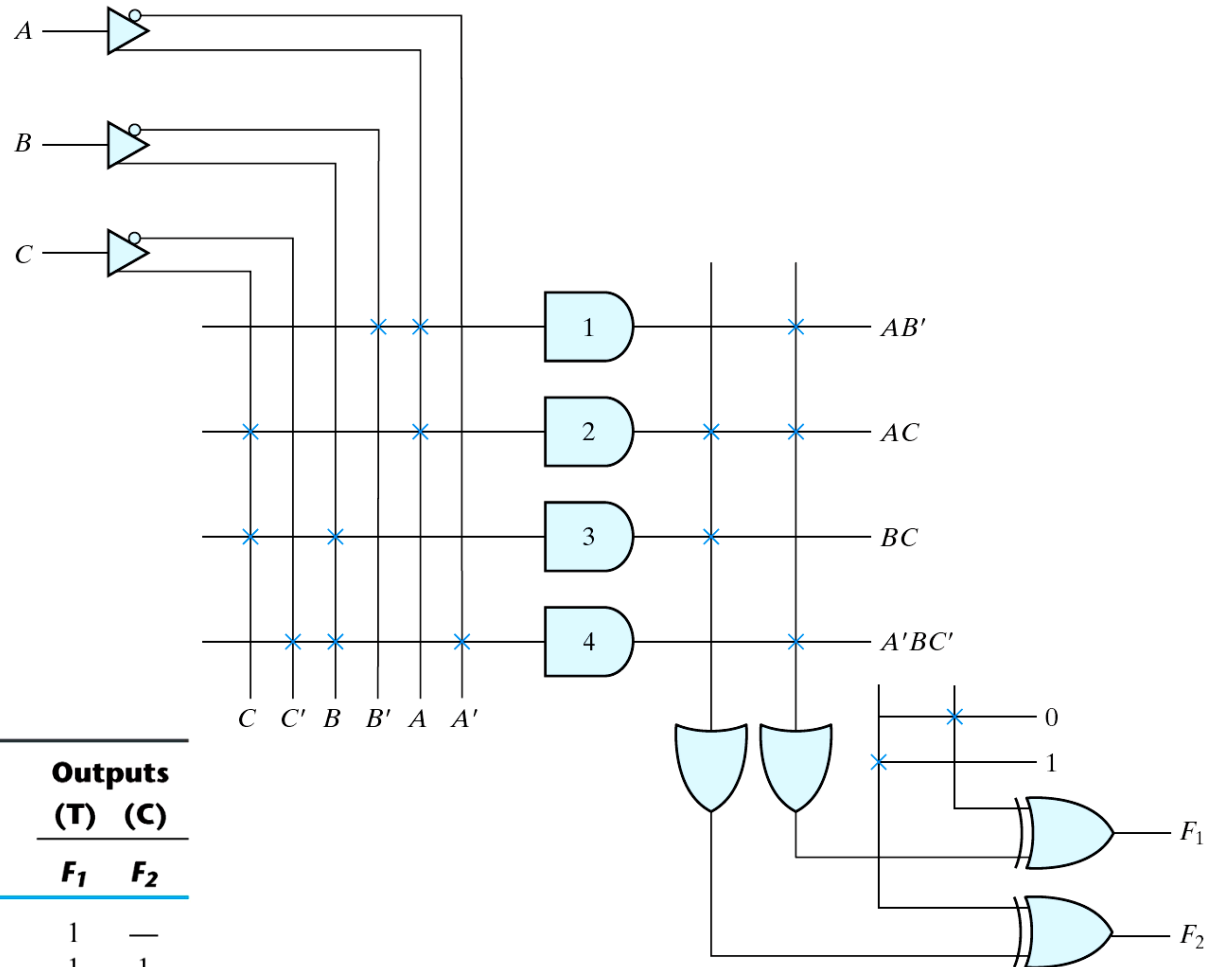


Table 7.5
PLA Programming Table

		Inputs			Outputs (T) (C)	
		A	B	C	F ₁	F ₂
AB'	1	1	0	—	1	—
AC	2	1	—	1	1	1
BC	3	—	1	1	—	1
A'BC'	4	0	1	0	1	—

Note: See text for meanings of dashes.

PLA Implementation (2/2) (p.338, 339)

■ The size of a PLA

- ◆ The number of inputs
- ◆ The number of product terms (AND gates)
- ◆ The number of outputs (OR gates)

■ PLA design issues

- ◆ Reduce the number of distinct product terms
- ◆ The number of literals in a product is not important

Examples 7.2 (1/2) (p.340)

■ $F_1(A, B, C) = \Sigma (0, 1, 2, 4)$

■ $F_2(A, B, C) = \Sigma (0, 5, 6, 7)$

- ◆ Both the true value and the complement of the function should be simplified to check

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0 1	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 0	m_6 0

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0 1	m_1 0	m_3 0	m_2 0
	1	m_4 0	m_5 1	m_7 1	m_6 1

Fig. 7.15 Solution to Example 7.2


Examples 7.2 (2/2) (p.341)

■ $F_1 = (AB + AC + BC)'$

■ $F_2 = AB + AC + A'B'C'$

PLA programming table

Product term		Inputs			Outputs	
		A	B	C	(C) F_1	(T) F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	–
$A'B'C'$	4	0	0	0	–	1

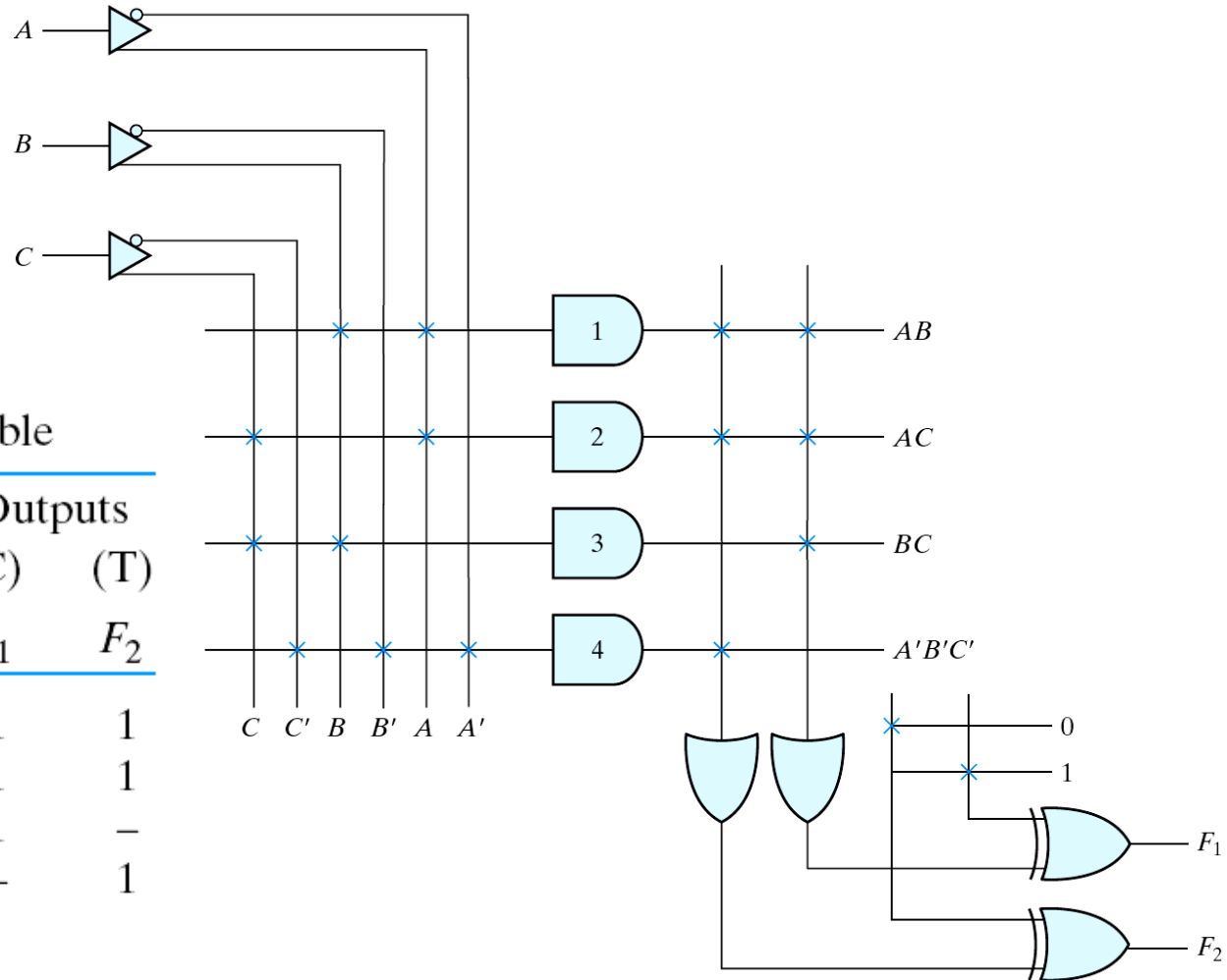

7-8 Sequential Programmable Devices

(p.345)

▣ Sequential programmable logic device

- ◆ SPLD
- ◆ PLD + flip-flops

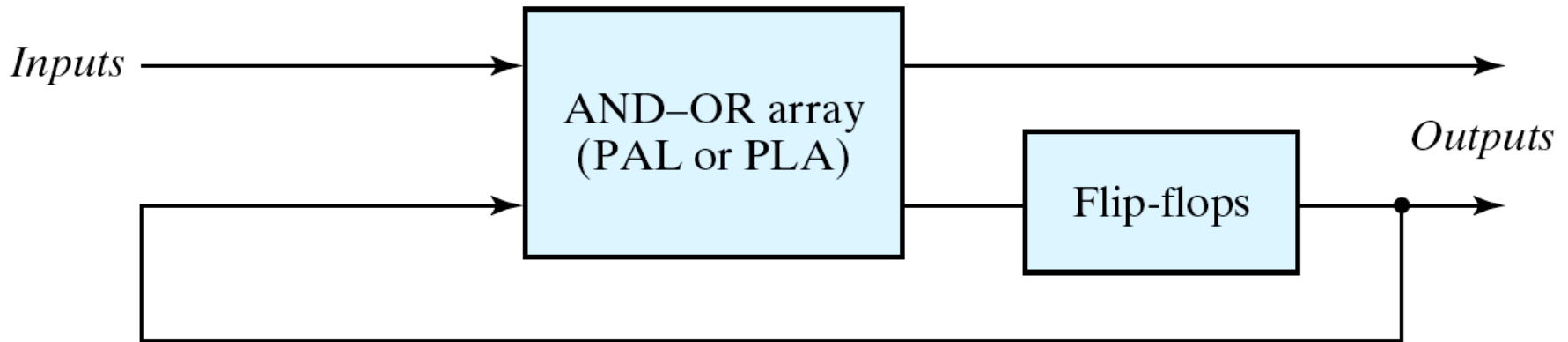


Fig. 7.18 Sequential programmable logic device

Complex PLD (p.347)

■ Complex PLD – CPLD

- ◆ Put a lot of PLDS on a chip
- ◆ Add wires between them whose connections can be programmed
- ◆ Use fuse/EEPROM technology

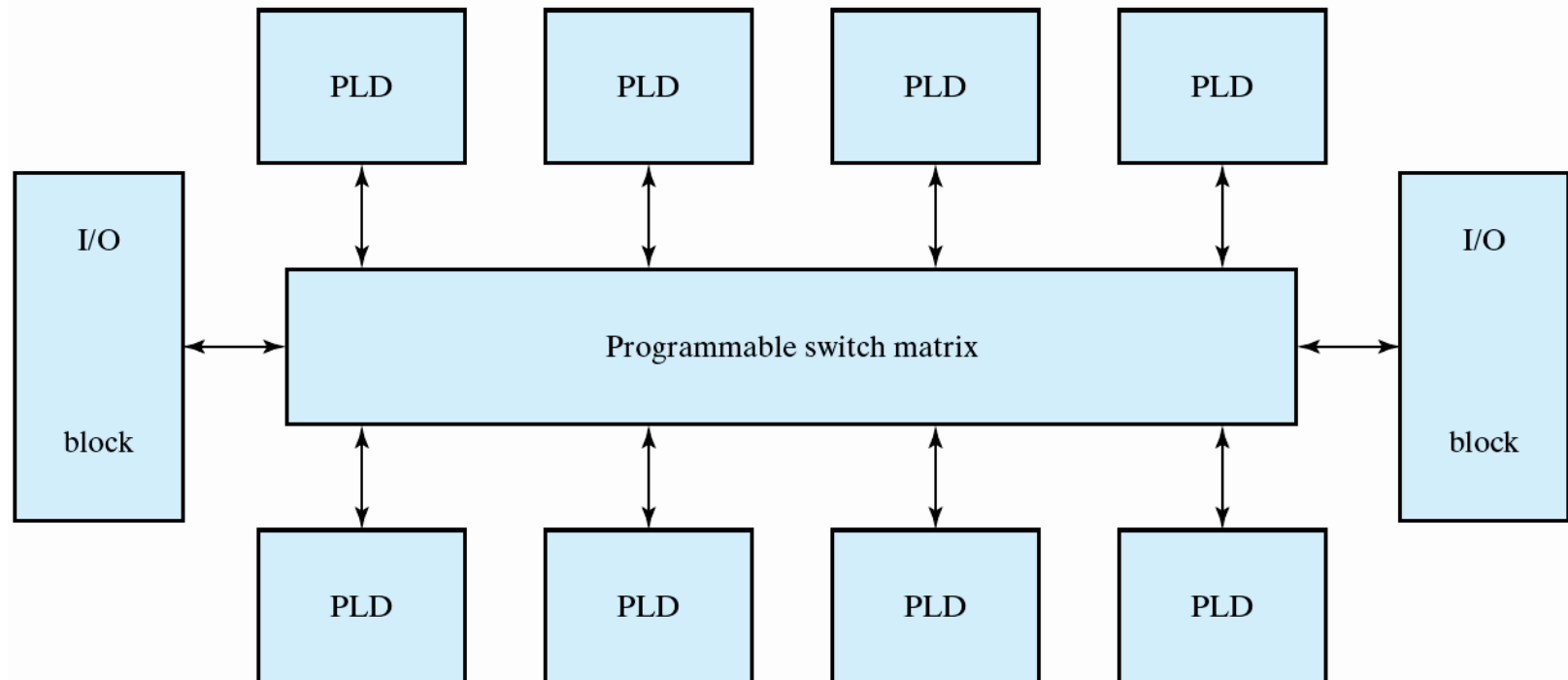


Fig. 7.20 General CPLD configuration

Field-Programmable Gate Arrays (p.349)

- **Configurable Logic blocks**
 - ◆ To implement combinational and sequential logic
- **Interconnect**
 - ◆ Wires to connect inputs and outputs to logic blocks
- **I/O blocks**
 - ◆ Special logic blocks at periphery of device for external connections
- **Key questions**
 - ◆ How to make logic blocks programmable?
 - ◆ How to connect the wires?

