

**CS204: 數位系統設計**

**Gate-Level Minimization**

---

# Outline of Chapter 3

---

- ▣ 3.1 Introduction
- ▣ 3.2 The Map Method
- ▣ 3.3 Four-Variable Map
- ▣ 3.4 Product-of-Sums Simplification
- ▣ 3.5 Don't-Care Conditions
- ▣ 3.6 NAND and NOR Implementation
- ▣ 3.7 Other Two-Level Implementation
- ▣ 3.8 Exclusive-OR Function
- ▣ 3.9 Hardware Description Language

# 3-1 Introduction (p.89)

- **Gate-level minimization** refers to the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit
- **The complexity of the digital logic gates**
  - ◆ The complexity of the algebraic expression
- **Algebraic approaches: lack specific rules**

# 3-2 The Map Method (p.89, 90)

## ■ The Karnaugh map

- ◆ A simple **and** straight forward procedure
- ◆ A pictorial form of a truth table
- ◆ Applicable if the # of variables  $\leq 6$

## ■ A diagram made up of squares

- ◆ Each square represents one minterm

# Two-Variable Map (p.90)

## ■ A two-variable map

- ◆ Four minterms
- ◆  $x' = \text{row } 0$ ;  $x = \text{row } 1$
- ◆  $y' = \text{column } 0$ ;  $y = \text{column } 1$
- ◆ A truth table in square diagram
- ◆ Fig. 3.2(a):  $xy = m_3$
- ◆ Fig. 3.2(b):  $x + y = x'y + xy' + xy = m_1 + m_2 + m_3$

 


Figure 3.1 Two-variable Map

# A Three-Variable Map (p.91)

## ■ A three-variable map

- ◆ Eight minterms
- ◆ The Gray code sequence
- ◆ Any two adjacent squares in the map differ by only one variable
  - » Primed in one square and unprimed in the other
  - » e.g.,  $m_5$  and  $m_7$  can be simplified
  - »  $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

(a)

		$y$			
		$yz$		11	10
$x$	0	00	01	$x'y'z$	$x'yz'$
	1	11	10	$xy'z$	$xyz'$
		$z$			

(b)

Figure 3.3 Three-variable Map

# A Three-Variable Map (p.91, 92)

- ◆  $m_0$  and  $m_2$  ( $m_4$  and  $m_6$ ) are adjacent
- ◆  $m_0 + m_2 = x'y'z' + x'yz' = x'z' (y' + y) = x'z'$
- ◆  $m_4 + m_6 = xy'z' + xyz' = xz' (y' + y) = xz'$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

(a)

		$y$			
		$yz$			
		00	01	11	10
$x$	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$x$	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$
		$z$			

(b)

Fig. 3-3 Three-variable Map

# Example 3.1 (p.92)

■ Example 3.1: simplify the Boolean function  $F(x, y, z) = \Sigma(2, 3, 4, 5)$

◆  $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 


Figure 3.4 Map for Example 3.1,  $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$



## Example 3.2 (p.93)

■ Example 3.2: simplify  $F(x, y, z) = \Sigma(3, 4, 6, 7)$

◆  $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$


 


Figure 3.5 Map for Example 3-2;  $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$


# Four adjacent Squares (p.94)
 
## Consider four adjacent squares

- ◆ 2, 4, and 8 squares
- ◆  $m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz' = x'z'(y' + y) + xz'(y' + y) = x'z' + xz' = z'$
- ◆  $m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz = x'z(y' + y) + xz(y' + y) = x'z + xz = z$



(a)

 

(b)

Figure 3.3 Three-variable Map

# Example 3.3 (p.94)

■ Example 3.3: simplify  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

◆  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

 


Figure 3.6 Map for Example 3-3,  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

## Example 3.4 (p.95)

■ Example 3.4: let  $F = A'C + A'B + AB'C + BC$

- a) Express it in sum of minterms
- b) Find the minimal sum of products expression

$$F(A, B, C) = \Sigma(1, 2, 3, 5, 7) = C + A'B$$

 


Figure 3.7 Map for Example 3.4,  $A'C + A'B + AB'C + BC = C + A'B$

# 3.3 Four-Variable Map (p.96)

## ■ The map

- ◆ 16 minterms
- ◆ Combinations of 2, 4, 8, and 16 adjacent squares

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)

$wx$	$yz$		$y$	
	00	01	11	10
00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$

(b)

Figure 3.8 Four-variable Map

# Example 3.5 (p.97)

- Example 3.5: simplify  $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$


 


Figure 3.9 Map for Example 3-5;  $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

# Example 3.6 (p.97, 98)

 Example 3.6: simplify  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$



Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$   
 $A'B'C' + AB'C' = B'C'$

Figure 3.9 Map for Example 3-6;  $A'B'C' + B'CD' + A'BCD' + AB'C' = B'D' + B'C' + A'CD'$

# Prime Implicants (p.98)

## □ K-map-based minimization

- ◆ All the minterms are covered
- ◆ Minimize the number of terms

## □ Prime Implicants

- ◆ A prime implicant: a product term obtained by combining the maximum possible number of adjacent squares (combining all possible maximum numbers of squares)
- ◆ Essential P.I.: **a prime implicant in which there exists a minterm which is only covered by the prime implicant**
- ◆ The essential P.I. must be included
  - » **So, select them first**




# Prime Implicants (p.99)

■ Consider  $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$


◆ The simplified expression may not be unique
 
$$\begin{aligned} F &= BD + B'D' + CD + AD = BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD = BD + B'D' + B'C + AB' \end{aligned}$$



Note:  $A'B'C'D' + A'B'CD' = A'B'D'$   
 $AB'C'D' + AB'CD' = AB'D'$   
 $A'B'D' + AB'D' = B'D'$

 (a) Essential prime implicants  
 $BD$  and  $B'D'$



(b) Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$

Figure 3.11 Simplification Using Prime Implicants

# 3-4 Product of Sums Simplification

(p.100)

## □ Approach #1

- ◆ Simplified  $F'$  in the form of sum of products
- ◆ Apply DeMorgan's theorem  $F = (F')'$
- ◆  $F'$ : sum of products  $\rightarrow F$ : product of sums


## □ Approach #2: duality

- ◆ Combinations of maxterms (it was minterms)
- ◆  $M_0 M_1 = (A+B+C+D)(A+B+C+D') = (A+B+C)+(DD') = A+B+C$

AB \ CD	CD			
	00	01	11	10
00	$M_0$	$M_1$	$M_3$	$M_2$
01	$M_4$	$M_5$	$M_7$	$M_6$
11	$M_{12}$	$M_{13}$	$M_{15}$	$M_{14}$
10	$M_8$	$M_9$	$M_{11}$	$M_{10}$

# Example 3.7 (p.101)

 - Example 3.7: simplify  $F = \Sigma(0, 1, 2, 5, 8, 9, 10)$  into (a) sum-of-products form, and (b) product-of-sums form:



Note:  $BC'D' + BCD' = BD'$

a)  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$


b)  $F' = AB + CD + BD'$

» Apply DeMorgan's theorem;  
 $F = (A' + B')(C' + D')(B' + D)$

Figure 3.12 Map for Example 3.7,  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$


## Example 3.7 (cont.) (p.102)
 
### Gate implementation of the function of Example 3.7



(a)  $F = B'D' + B'C' + A'C'D$

**Sum-of products form**

 

(b)  $F = (A' + B')(C' + D')(B' + D)$

**Product-of sums form**


Figure 3.13 Gate Implementation of the Function of Example 3.7

# 3-5 Don't-Care Conditions (p.104)


- The value of a function is not specified for certain combinations of variables
  - ◆ BCD; 1010-1111: don't care
- The don't-care conditions can be utilized in logic minimization
  - ◆ Can be implemented as 0 or 1
- Example 3.8: simplify  $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$  which has the don't-care conditions  $d(w, x, y, z) = \Sigma(0, 2, 5)$
 
# Example 3.8 (cont.) (p.104, 105)

- ◆  $F = yz + w'x'$ ;  $F = yz + w'z$
- ◆  $F = \Sigma(0, 1, 2, 3, 7, 11, 15)$ ;  $F = \Sigma(1, 3, 5, 7, 11, 15)$
- ◆ Either expression is acceptable



(a)  $F = yz + w'x'$

 

(b)  $F = yz + w'z$

Figure 3.15 Example with don't-care Conditions

# 3-6 NAND and NOR Implementation (p.106)

■ NAND gate is a **universal** gate

◆ Can implement any Boolean function

 


Figure 3.16 Logic Operations with NAND Gates

# NAND Gate (p.107)

## ■ Two graphic symbols for a NAND gate

 


Figure 3.17 Two Graphic Symbols for NAND Gate



# Two-level Implementation (p.107, 108)

## Two-level logic

- ◆ NAND-NAND = sum of products
- ◆ Example:  $F = AB + CD$
- ◆  $F = ((AB)' (CD)')' = AB + CD$

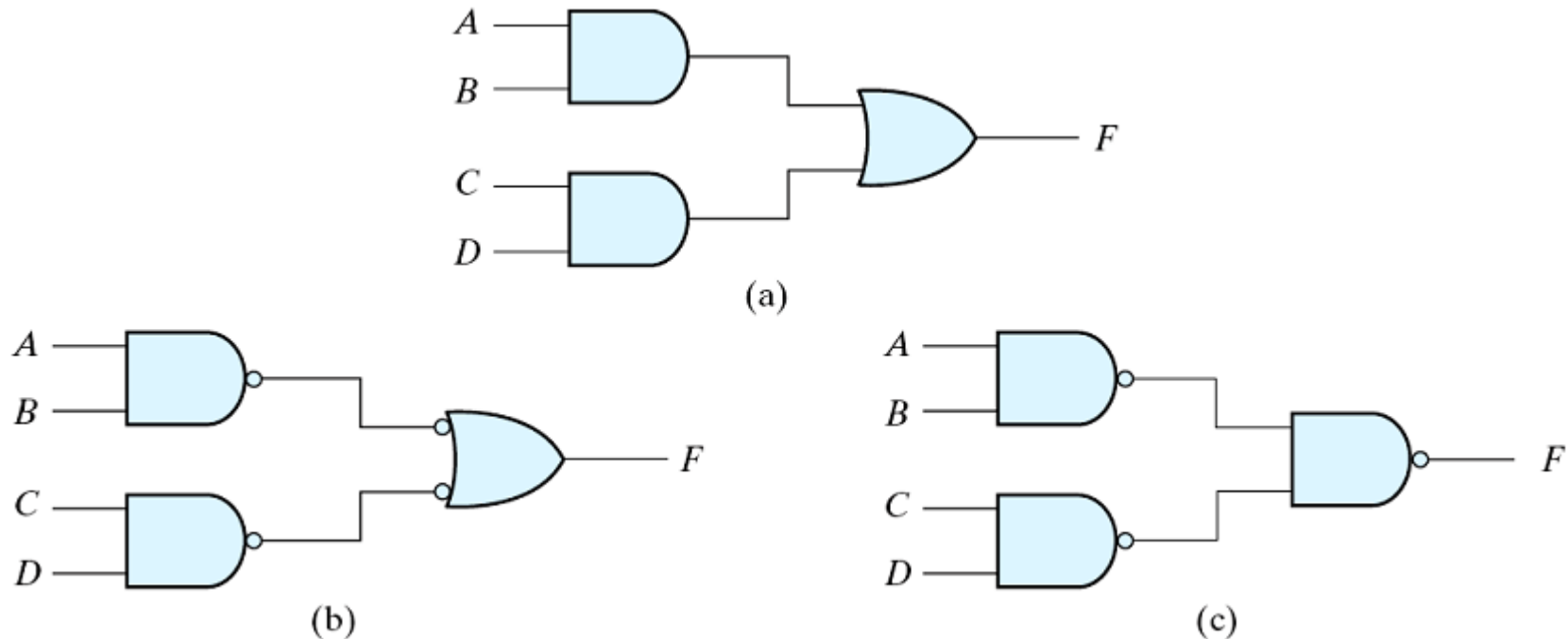


Figure 3.18 Three ways to implement  $F = AB + CD$

# Example 3.9 (p.108, 109)

■ Example 3-9: implement  $F(x, y, z) =$

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7) \longrightarrow F(x, y, z) = xy' + x'y + z$$

 


Figure 3.19 Solution to Example 3-9

# Procedure with Two Levels NAND (p.109)

## □ The procedure


- ◆ Simplified in the form of sum of products;
- ◆ A NAND gate for each product term; the inputs to each NAND gate are the literals of the term (the first level);
- ◆ A single NAND gate for the second sum term (the second level);
- ◆ A term with a single literal requires an inverter in the first level

# Multilevel NAND Circuits (p.109, 110)


## ■ Boolean function implementation
 
### ◆ AND-OR logic → NAND-NAND logic

- » AND → NAND + inverter
- » OR: inverter + OR = NAND



 
(a) AND-OR gates **Alternating levels of AND and OR gates**




(b) NAND gates

Figure 3.20 Implementing  $F = A(CD + B) + BC'$

# NAND Implementation (p.110, 111)

 

(a) AND-OR gates

 

(b) NAND gates

Figure 3.21 Implementing  $F = (AB' + A'B)(C + D')$

# NOR Implementation (p.111, 112)

- NOR function is the dual of NAND function
- The NOR gate is also universal


 



Figure 3.22 Logic Operation with NOR Gates

# Two Graphic Symbols for a NOR Gate

(p.112, 113)

 

(a) OR-invert

 

(b) Invert-AND

Figure 3.23 Two Graphic Symbols for NOR Gate

Example:  $F = (A + B)(C + D)E$

 


Figure 3.24 Implementing  $F = (A + B)(C + D)E$

# Example (p.113)

Example:  $F = (AB' + A'B)(C + D')$

 


Figure 3.25 Implementing  $F = (AB' + A'B)(C + D')$  with NOR gates



# 3-7 Other Two-level Implementations

## ■ 16 possible combinations of two-level forms

### ◆ Eight of them: degenerate forms = a single operation

- » AND-AND, AND-NAND, OR-OR, OR-NOR, NAND-OR, NAND-NOR, NOR-AND, NOR-NAND.

### ◆ The eight non-degenerate forms

- » AND-OR, OR-AND, NAND-NAND, NOR-NOR, NOR-OR, NAND-AND, OR-NAND, AND-NOR.
- » **AND-OR** and **NAND-NAND** = sum of products
- » **OR-AND** and **NOR-NOR** = product of sums
- » **NAND-AND** and **AND-NOR** = AND-OR-INVERT
- » **NOR-OR** and **OR-NAND** = OR-AND-INVERT

# AND-OR-Invert Implementation (p.115)

## ■ AND-OR-INVERT (AOI) Implementation

- ◆ **NAND-AND = AND-NOR = AOI**
- ◆  **$F = (AB+CD+E)'$  (sum of products + Inverter)**
- ◆  **$F' = AB+CD+E$  (sum of products)**


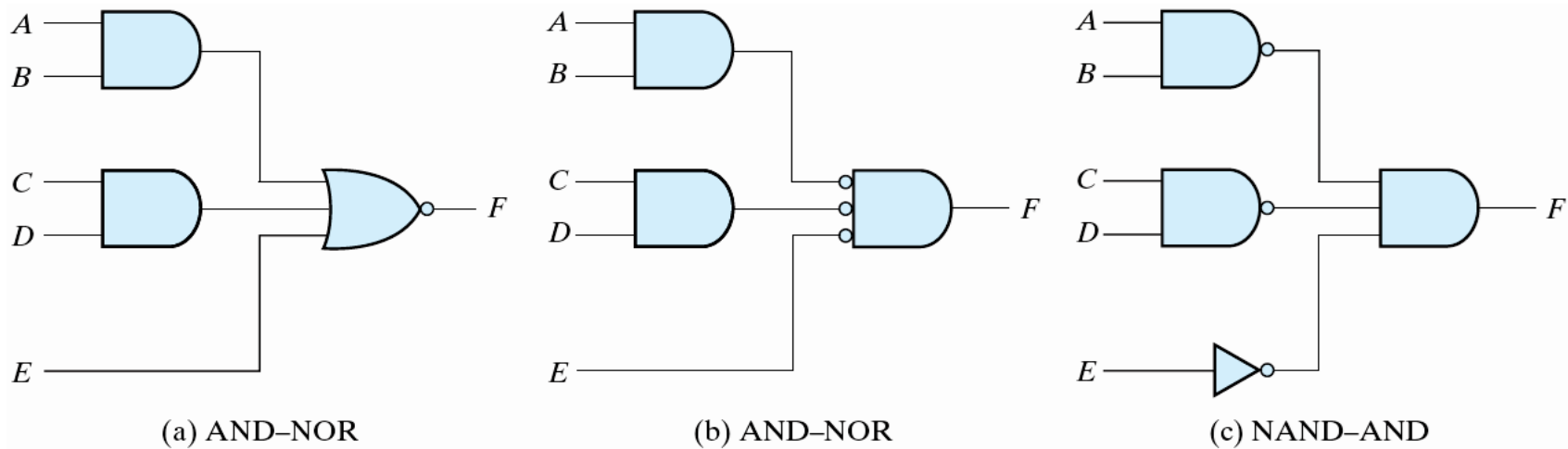


Figure 3.27 AND-OR-INVERT circuits,  $F = (AB + CD + E)'$


# OR-AND-Invert Implementation (p.116)
 
## OR-AND-INVERT (OAI) Implementation


- ◆ OR-NAND = NOR-OR = OAI
- ◆  $F = ((A+B)(C+D)E)'$  (product of sums + Inverter)
- ◆  $F' = (A+B)(C+D)E$  (product of sums)



(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

Figure 3.28 OR-AND-INVERT circuits,  $F = ((A+B)(C+D)E)'$

# Tabular Summary and Examples (p.117)


**Table 3.2**  
*Implementation with Other Two-Level Forms*

<b>Equivalent Nondegenerate Form</b>		<b>Implements the Function</b>	<b>Simplify <math>F'</math> into</b>	<b>To Get an Output of</b>
<b>(a)</b>	<b>(b)*</b>			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	$F$

\*Form (b) requires an inverter for a single literal term.

# Tabular Summary and Examples (p.117)

 - Example 3-10: Implement the following function with  
(a) AND-NOR (b) NAND-AND (c) OR-NAND (d) NOR-OR forms



(a) Map simplification in sum of products

# Tabular Summary and Examples (p.118)


## ▣ (a) AND-NOR (b) NAND-AND

◆  $F' = x'y + xy' + z$


( $F'$ : sum of products)

◆  $F = (x'y + xy' + z)'$

( $F$ : AOI implementation)

 

AND-NOR

 

NAND-AND

(b)  $F = (x'y + xy' + z)'$



# Tabular Summary and Examples (p.118)

## ■ (c) OR-NAND (d) NOR-OR forms

◆  $F = x'y'z' + xyz'$  ( $F$ : sum of products)

◆  $F' = (x+y+z)(x'+y'+z)$  ( $F'$ : product of sums)

  ◆  $F = ((x+y+z)(x'+y'+z))'$  ( $F$ : OAI)



(c)  $F = [(x + y + z) (x' + y' + z)]'$

# 3-8 Exclusive-OR Function (p.119)

## ■ Exclusive-OR (XOR)

- ◆  $x \oplus y = xy' + x'y$

## ■ Exclusive-NOR (XNOR)

- ◆  $(x \oplus y)' = xy + x'y'$

## ■ Some identities

- ◆  $x \oplus 0 = x$

- ◆  $x \oplus 1 = x'$

- ◆  $x \oplus x = 0$

- ◆  $x \oplus x' = 1$

- ◆  $x \oplus y' = (x \oplus y)'$

- ◆  $x' \oplus y = (x \oplus y)'$

## ■ Commutative and associative

- ◆  $A \oplus B = B \oplus A$


- ◆  $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$




# Exclusive-OR Implementations (p.120)
 
## ■ Implementations

◆  $(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Figure 3.30 Exclusive-OR Implementations

# Odd Function (p.120, 121)

- ◆  $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C = AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$
- ◆ XOR is an odd function  $\rightarrow$  an odd number of 1's, then  $F = 1$
- ◆ XNOR is an even function  $\rightarrow$  an even number of 1's, then  $F = 1$

		$B$			
		$BC$		00	01
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
			1		1
		1		1	

Diagram (a) shows a 2x4 Karnaugh map for the odd function  $F = A \oplus B \oplus C$ . The map is labeled with variables  $A$ ,  $B$ , and  $C$ . The top row corresponds to  $A=0$  and the bottom row to  $A=1$ . The columns correspond to  $BC$  values 00, 01, 11, and 10. The cells are labeled  $m_0, m_1, m_3, m_2$  for  $A=0$  and  $m_4, m_5, m_7, m_6$  for  $A=1$ . The function value is 1 in cells  $m_1, m_2, m_4, m_7$ , which are grouped by a bracket labeled  $C$  under the bottom row.

(a) Odd function  $F = A \oplus B \oplus C$


		$B$			
		$BC$		00	01
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		1		1	
			1		1

(b) Even function  $F = (A \oplus B \oplus C)'$


Figure 3.31 Map for a Three-variable Exclusive-OR Function

# XOR and XNOR (p.121)
 
## ■ Logic diagram of odd and even functions



(a) 3-input odd function

 

(b) 3-input even function

Figure 3.32 Logic Diagram of Odd and Even Functions

# Four-variable Exclusive-OR function

## Four-variable Exclusive-OR function

$$\begin{aligned} A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) = \\ &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C'D) \end{aligned}$$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$	$m_{13}$ 1	$m_{15}$	$m_{14}$ 1
	10	$m_8$ 1	$m_9$	$m_{11}$ 1	$m_{10}$

(a) Odd function  $F = A \oplus B \oplus C \oplus D$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$	$m_{15}$ 1	$m_{14}$
	10	$m_8$	$m_9$ 1	$m_{11}$	$m_{10}$ 1

(b) Even function  $F = (A \oplus B \oplus C \oplus D)'$

Figure 3.33 Map for a Four-variable Exclusive-OR Function

# Parity Generation and Checking (p.122, 123)

## ■ Parity Generation and Checking

- ◆ A parity bit:  $P = x \oplus y \oplus z$
- ◆ Parity check:  $C = x \oplus y \oplus z \oplus P$ 
  - »  $C=1$ : one bit error or an odd number of data bit error
  - »  $C=0$ : correct or an even # of data bit error

 


Figure 3.34 Logic Diagram of a Parity Generator and Checker

# Parity Generation and Checking

**Table 3.3**

*Even-Parity-Generator Truth Table*

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Parity Generation and Checking (p.124)

**Table 3.4**  
*Even-Parity-Checker Truth Table*

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0